

#### TECH BULLETIN

TECHNICAL BULLETIN Distribution: Installers

© 120CT20 Clare Controls, LLC.

# Clare Video Doorbell: Using 2 Doorbells with a Single Transformer and Chime


Last modified: 10/12/20

## Introduction

Use this document as a guide for wiring two v3 Clare Video Doorbells (CLR-CVP-B3DB50-ODIW) to a single transformer and chime.

Note: The transformer must be 24V and rated for a minimum of 30W.

Figure 1: Front and rear doorbell connection

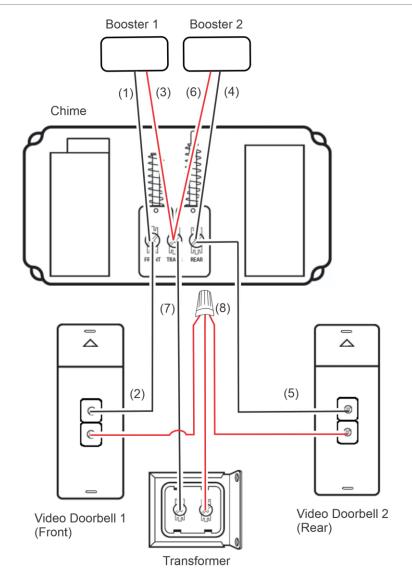

DOC ID - 1997 • Rev 01 1 / 2

#### To wire the doorbells:

- 1. Wire one lead from the first booster and first doorbell (Front) to the Front chime terminal (1 and 2).
- 2. Wire the second lead of the first booster to the chime's TRANS terminal (3).
- 3. Wire one lead from the second booster and the second doorbell (Rear) to the REAR chime terminal (4 and 5).
- 4. Wire the second lead of the second booster to the chime's TRANS connector (6).
- 5. Terminate one of the transformer's wire to the chime's TRANS connector (7).
- 6. Terminate the wire from both the Front and Rear doorbells to the transformer's second termination post (8).

### Contact information

Clare Controls, LLC. 7519 Pennsylvania Ave, Suite 104 Sarasota, FL 34243

General: 941.328.3991 Fax: 941.870.9646 www.clarecontrols.com

Integrator/Dealer Support: 941.404.1072

claresupport@clarecontrols.com

Homeowner Support (ClareCare): 941.315.2273 (CARE)

help@clarecontrols.com